

Buck Converter Simulation Results

Daniela L. - July 29, 2025

Summary:

Simulation results of a Buck Converter tested in LTspice. Metrics include efficiency, output voltage, and ripple.

Simulation Results:

- Input Voltage (V_{in}): 12 V
- Load Resistance (R_{load}): 10 Ω
- Output Voltage (avg): 5.0897 V
- Output Current (avg): 0.509 A
- Output Power (P_{out}): 2.599 W
- Input Power (P_{in}): 3.0097 W
- Efficiency: 86.37%
- Switching Period (T): 9.969 μs
- Switching Frequency (f_{sw}): 100.304 kHz

Output Voltage Ripple:

- V_{max} : 5.1358 V
- V_{min} : 5.1066 V
- $\Delta V_{ripple} = V_{max} - V_{min} = 0.0292$ V
- Ripple % = $(0.0292 / 5.0897) * 100 \approx 0.574\%$

Conclusion:

The Buck Converter met design targets with high efficiency and low ripple, achieved in 3 days.